

COMP 122/L Lecture 19

Kyle Dewey

Overview

- Circuit minimization
 - Boolean algebra
 - Karnaugh maps

Circuit Minimization

Motivation

- Unnecessarily large programs: bad
- Unnecessarily large circuits: Very Bad™
 - Why?

Motivation

- Unnecessarily large programs: bad
- Unnecessarily large circuits: Very Bad™
 - Why?
 - Bigger circuits = bigger chips = higher cost (non-linear too!)
 - Longer circuits = more time needed to move electrons through = slower

Simplification

- Real-world formulas can often be simplified, according to algebraic rules
 - How might we simplify the following?

$$R = A * B + !A * B$$

-How might we simplify this?

Simplification

- Real-world formulas can often be simplified, according to algebraic rules
 - How might we simplify the following?

$$R = A * B + !A * B$$

$$R = B (A + !A)$$

$$R = B (\text{true})$$

$$R = B$$

Simplification Trick

- Look for products that differ only in one variable
 - One product has the original variable (A)
 - The other product has the other variable (\bar{A})

$$R = A * B + \bar{A} * B$$

Additional Example 1

$!ABCD + ABCD + !AB!CD + AB!CD$

Additional Example 1

$!ABCD + ABCD + !AB!CD + AB!CD$

$BCD(A + !A) + !AB!CD + AB!CD$

Additional Example 1

$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$

$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$

$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$

Additional Example 1

$!ABCD + ABCD + !AB!CD + AB!CD$

$BCD(A + !A) + !AB!CD + AB!CD$

$BCD + !AB!CD + AB!CD$

$BCD + B!CD(!A + A)$

Additional Example 1

$!ABCD + ABCD + !AB!CD + AB!CD$

$BCD(A + !A) + !AB!CD + AB!CD$

$BCD + !AB!CD + AB!CD$

$BCD + B!CD(!A + A)$

$BCD + B!CD$

Additional Example 1

$$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + B\overline{C}D(\overline{A} + A)$$
$$BCD + B\overline{C}D$$
$$BD(C + \overline{C})$$

Additional Example 1

$$\overline{A}BCD + ABCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD(A + \overline{A}) + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + \overline{A}B\overline{C}D + AB\overline{C}D$$
$$BCD + B\overline{C}D(\overline{A} + A)$$
$$BCD + B\overline{C}D$$
$$BD(C + \overline{C})$$

BD

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

$!A!BC + A!BC + A!B!C + !ABC + !AB!C$

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

$!A!BC + A!BC + A!B!C + !ABC + !AB!C$

$!BC(A + !A) + A!B!C + !ABC + !AB!C$

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

$!A!BC + A!BC + A!B!C + !ABC + !AB!C$

$!BC(A + !A) + A!B!C + !ABC + !AB!C$

$!BC + A!B!C + !ABC + !AB!C$

Additional Example 2

$$!A!BC + A!B!C + !ABC + !AB!C + A!BC$$

$$!A!BC + A!BC + A!B!C + !ABC + !AB!C$$

$$!BC(A + !A) + A!B!C + !ABC + !AB!C$$

$$!BC + A!B!C + !ABC + !AB!C$$

$$!BC + A!B!C + !AB(C + !C)$$

Additional Example 2

$!A!BC + A!B!C + !ABC + !AB!C + A!BC$

$!A!BC + A!BC + A!B!C + !ABC + !AB!C$

$!BC(A + !A) + A!B!C + !ABC + !AB!C$

$!BC + A!B!C + !ABC + !AB!C$

$!BC + A!B!C + !AB(C + !C)$

$!BC + A!B!C + !AB$

De Morgan's Laws

Also potentially useful for simplification

De Morgan's Laws

Also potentially useful for simplification

$$\neg (A + B) = \neg A \neg B$$

De Morgan's Laws

Also potentially useful for simplification

$$\neg (A + B) = \neg A \neg B$$

$$\neg (AB) = \neg A + \neg B$$

De Morgan Example

$$\neg (X + Y) \neg (\neg X + Z)$$

De Morgan Example

$$\neg (X + Y) \neg (!X + Z)$$

$\neg A$

$\neg B$

Has the overall form of $\neg A \neg B$

De Morgan Example

$$\neg (X + Y) \neg (\neg X + Z)$$

$\neg A$

$\neg B$

Has the overall form of $\neg A \neg B$

De Morgan Example

$$\neg (X + Y) \neg (\neg X + Z)$$

$\neg A$

$\neg B$

From De Morgan's Law:

$$\neg (A + B) = \neg A \neg B$$

Has the overall form of $\neg A \neg B$

De Morgan Example

$$\neg (X + Y) \neg (!X + Z)$$

$\neg A$

$\neg B$

From De Morgan's Law:

$$\neg (A + B) = \neg A \neg B$$

$$\neg (X + Y + !X + Z)$$

Has the overall form of $\neg A \neg B$

De Morgan Example

$$\neg (X + Y) \neg (!X + Z)$$

$\neg A$

$\neg B$

From De Morgan's Law:

$$\neg (A + B) = \neg A \neg B$$

$$\neg (X + Y + !X + Z)$$

$$\neg (X + \color{red}{!X} + \color{red}{Y} + Z)$$

Has the overall form of $\neg A \neg B$

De Morgan Example

$$\neg (X + Y) \neg (!X + Z)$$

$\neg A$

$\neg B$

From De Morgan's Law:

$$\neg (A + B) = \neg A \neg B$$

$$\neg (X + Y + !X + Z)$$

$$\neg (X + !X + Y + Z)$$

$$\neg (\text{true} + Y + Z)$$

De Morgan Example

$$\neg (X + Y) \neg (!X + Z)$$

$\neg A$

$\neg B$

From De Morgan's Law:

$$\neg (A + B) = \neg A \neg B$$

$$\neg (X + Y + !X + Z)$$

$$\neg (X + !X + Y + Z)$$

$$\neg (\text{true} + Y + Z)$$

$$\neg (\text{true})$$

De Morgan Example

$$\neg (X + Y) \neg (!X + Z)$$
$$!A$$
$$!B$$

From De Morgan's Law:

$$\neg (A + B) = \neg A \neg B$$
$$\neg (X + Y + !X + Z)$$
$$\neg (X + !X + Y + Z)$$
$$\neg (\text{true} + Y + Z)$$
$$\neg (\text{true})$$

false

Scaling Up

- Performing this sort of algebraic manipulation by hand can be tricky
- We can use *Karnaugh maps* to make it immediately apparent as to what can be simplified

Example

$$R = A * B + !A * B$$

-Start with the sum of products

Example

$$R = A * B + !A * B$$


A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

-Build the truth table

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

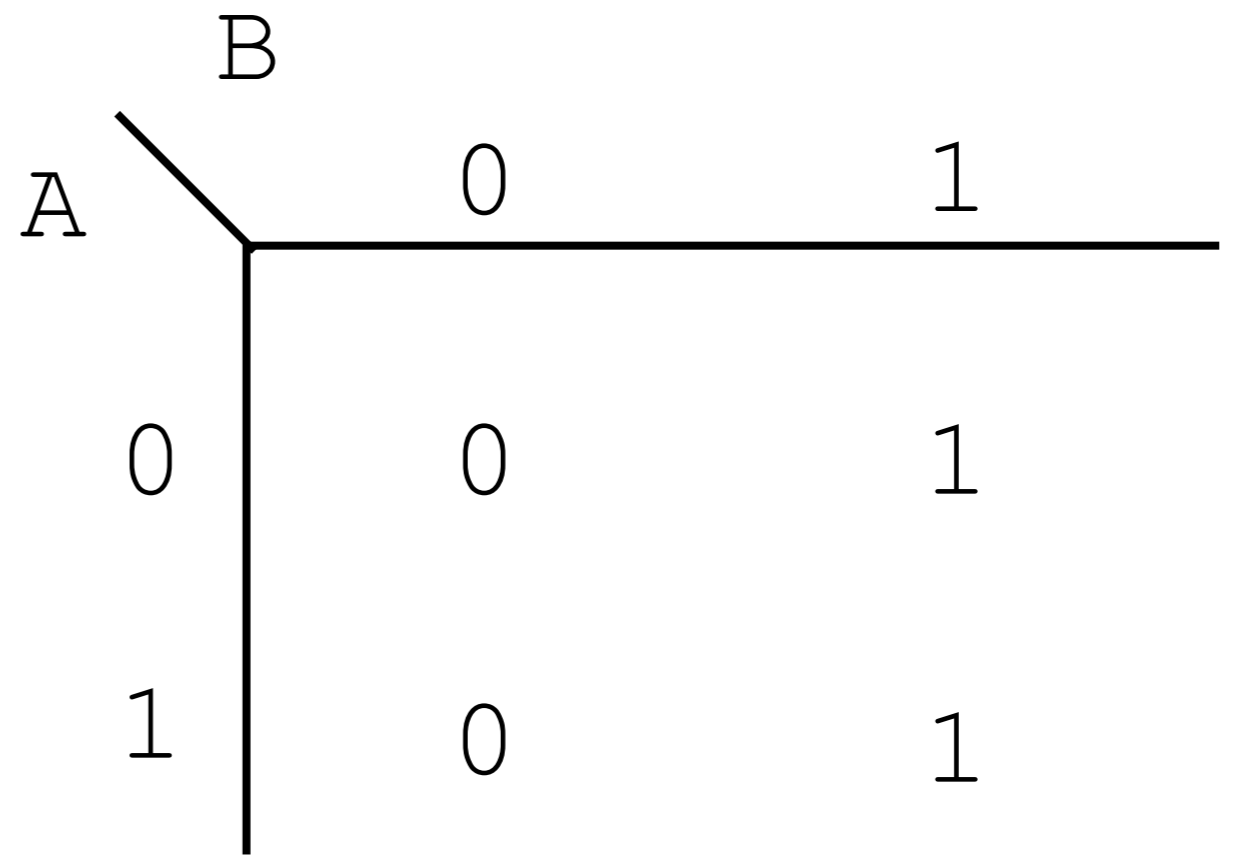


-Build the K-map

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

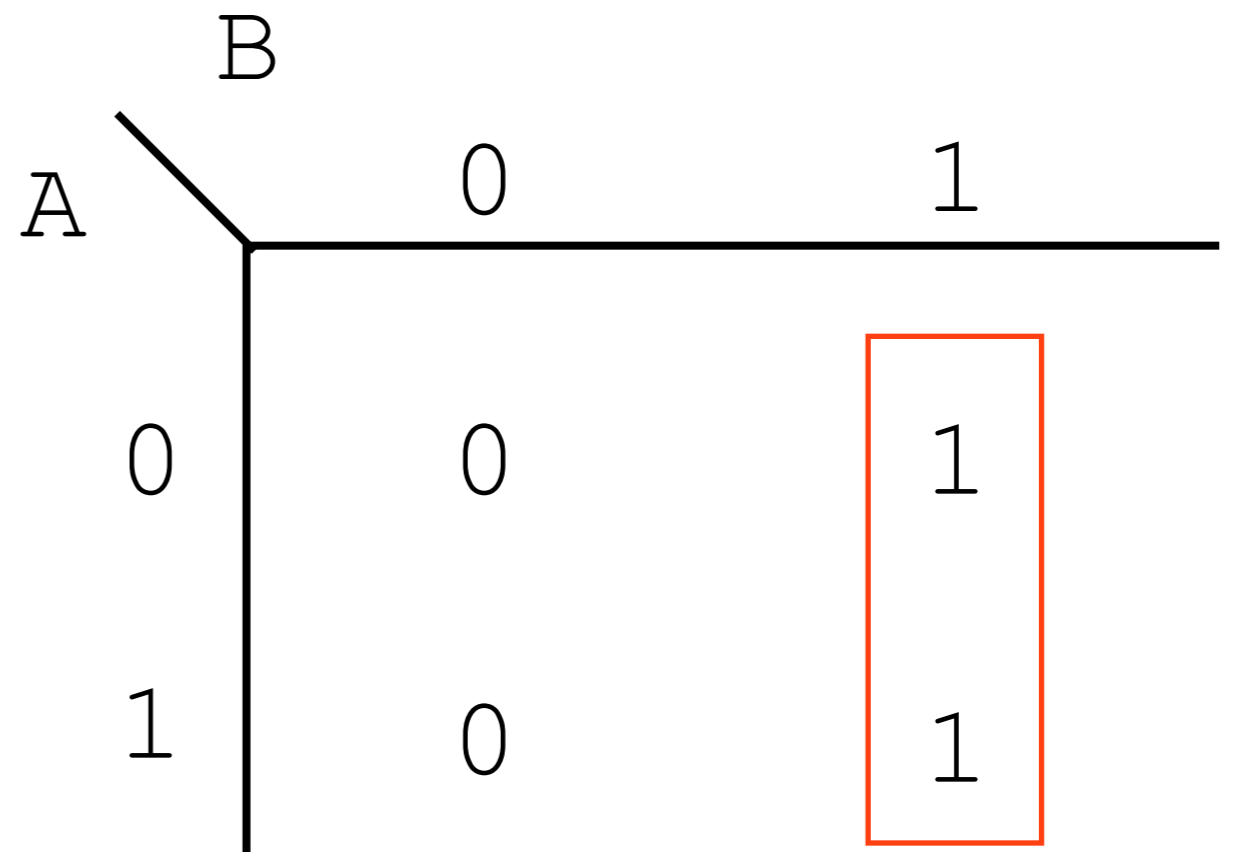


-Group adjacent (row or column-wise, NOT diagonal) 1's in powers of two (groups of 2, 4, 8...)

-

Example

$$R = A * B + !A * B$$

A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

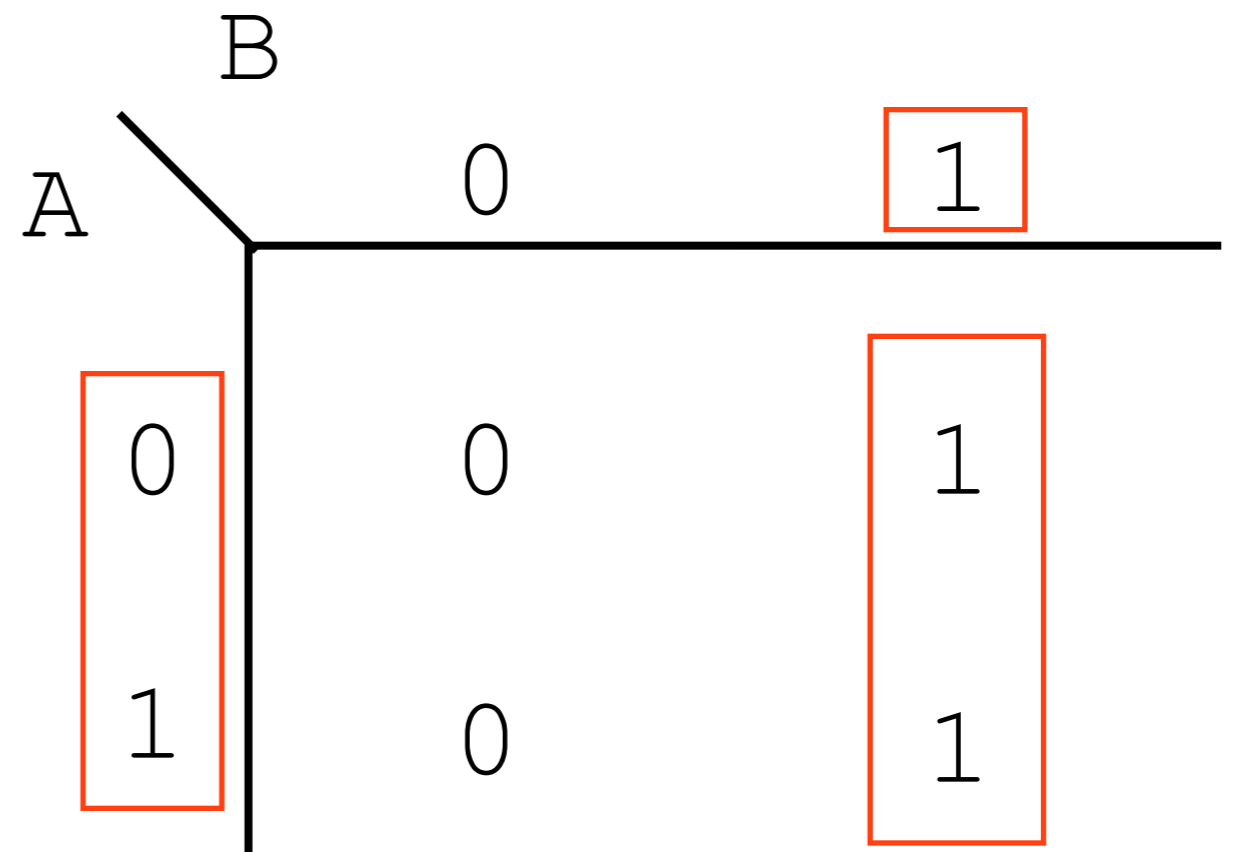


- The values that stay the same are saved, the rest are discarded
- This works because this means that the inputs that differ are irrelevant to the final value, and so they can be removed

Example

$$R = A * B + !A * B$$


A	B	O
0	0	0
0	1	1
1	0	0
1	1	1

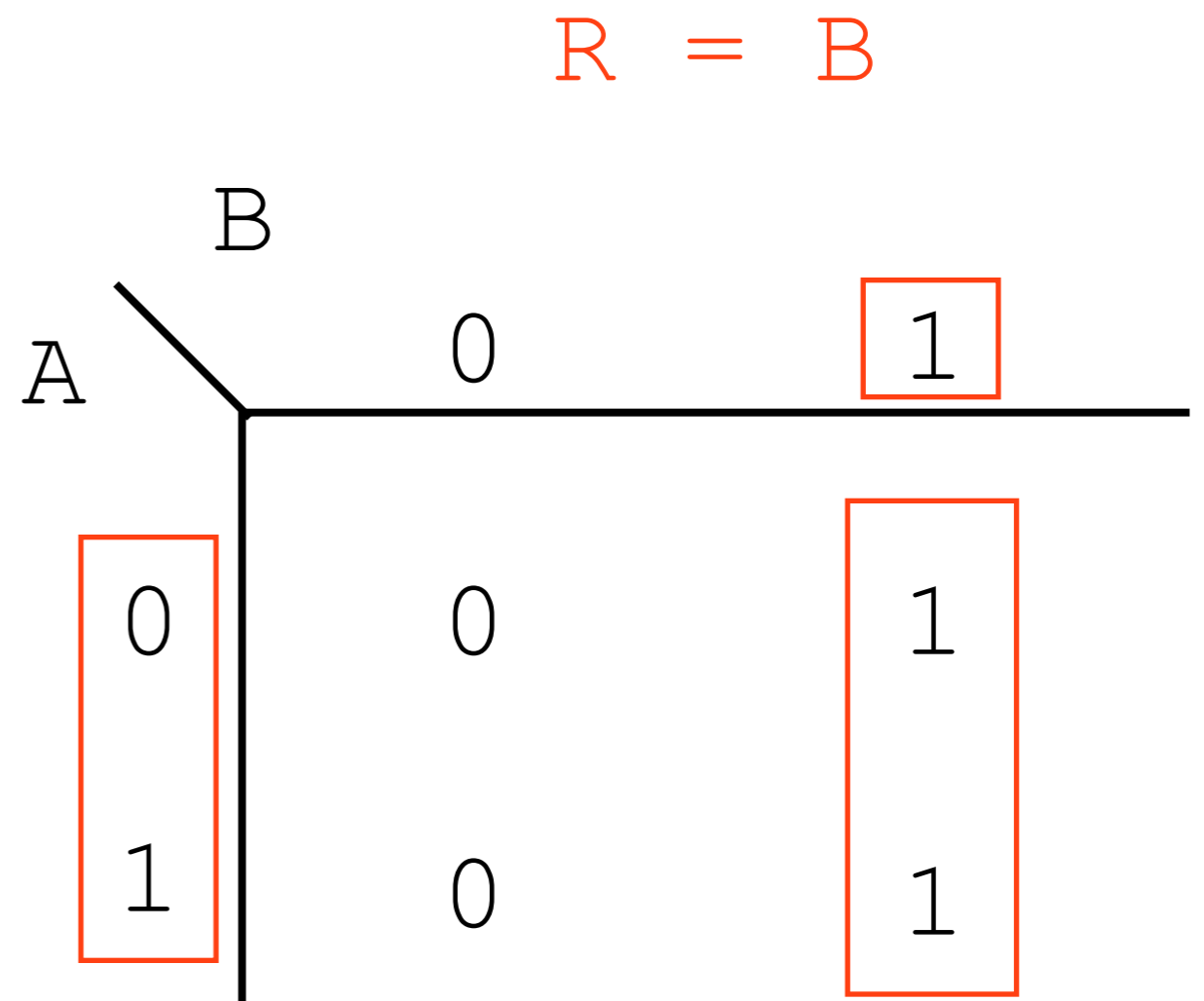

- The values that stay the same are saved, the rest are discarded
- This works because this means that the inputs that differ are irrelevant to the final value, and so they can be removed

Three Variables

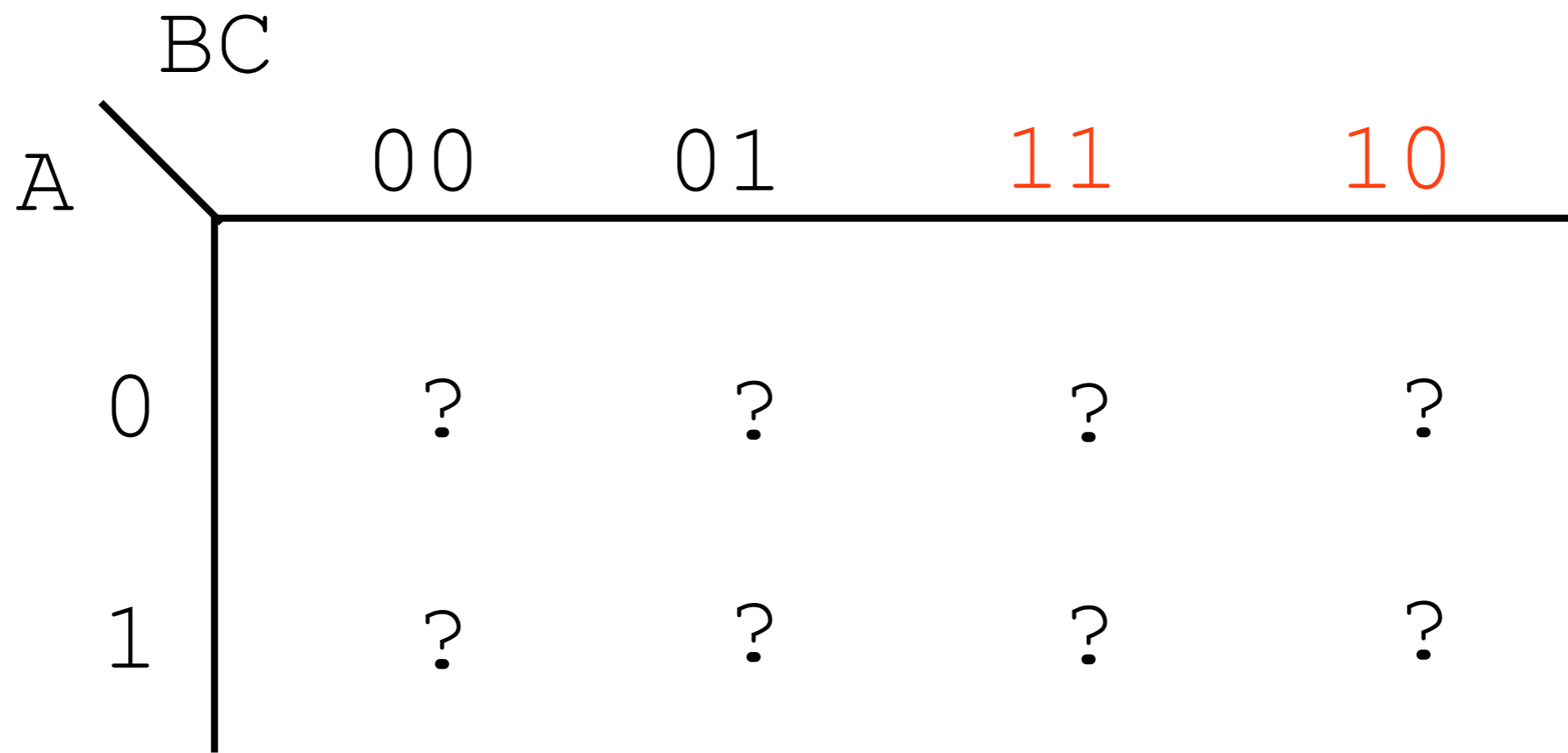- We can scale this up to three variables, by combining two variables on one axis
- The combined axis must be arranged such that only one bit changes per position



Three Variable Example

$$R = !A!BC + !ABC + A!BC + ABC$$

-Start with this formula


$$R = \neg A \neg B C + \neg A B C + A \neg B C + A B C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

-Build the truth table

$$R = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$


A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

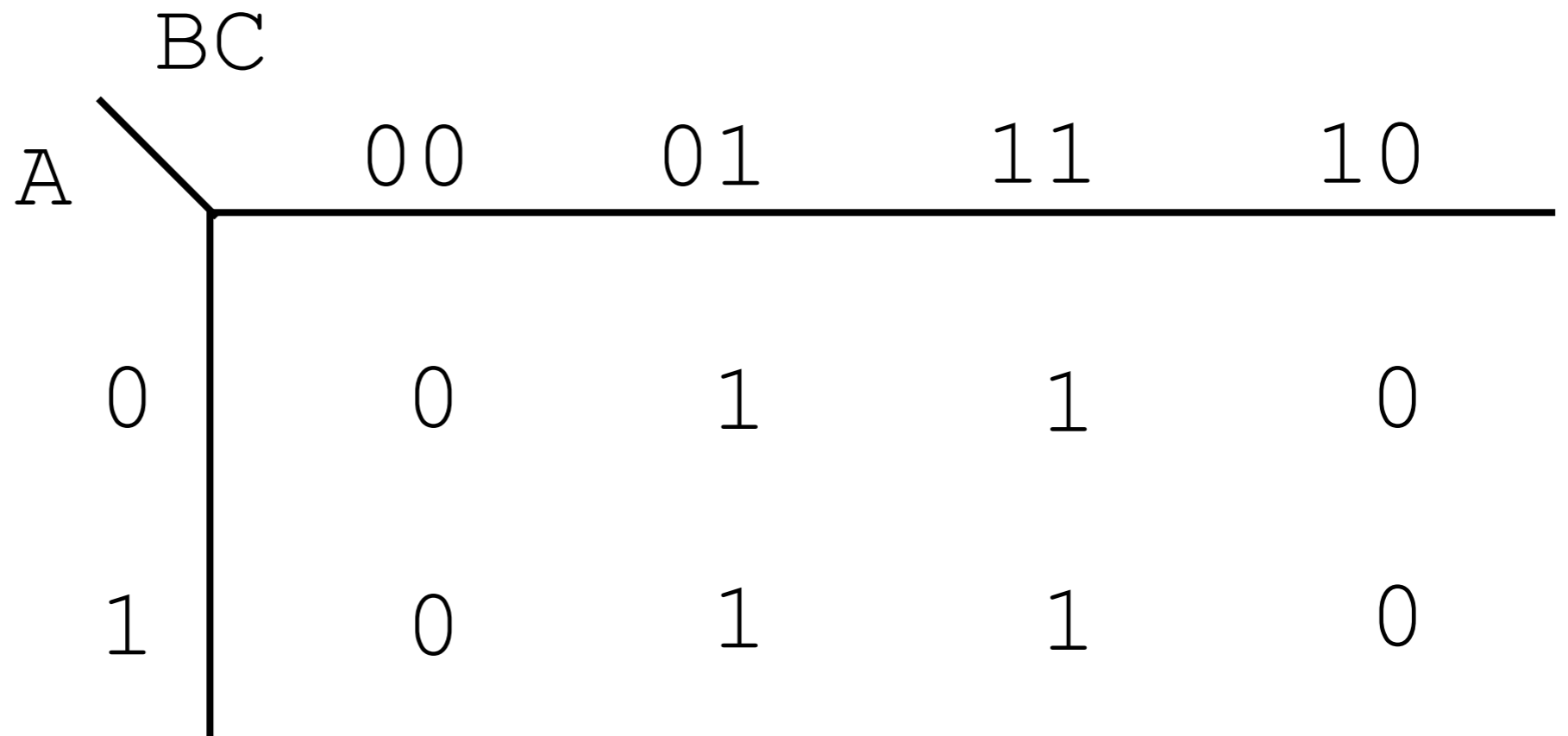

-Build the K-map

$$R = !A!BC + !ABC + A!BC + ABC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

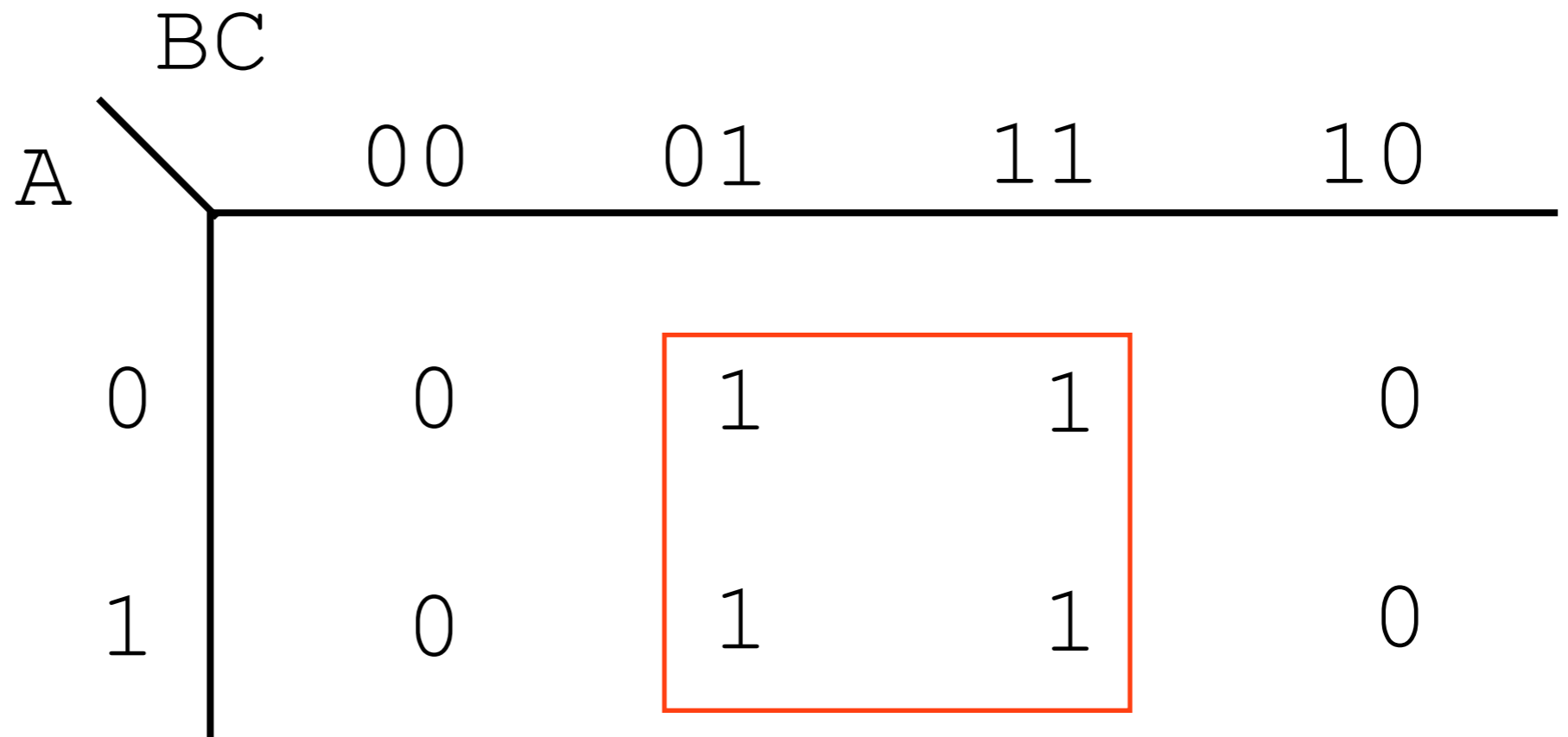


- Select the biggest group possible, in this case a square
- In order to get the most minimal circuit, we must always select the biggest groups possible

$$R = !A!BC + !ABC + A!BC + ABC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$R = C$$

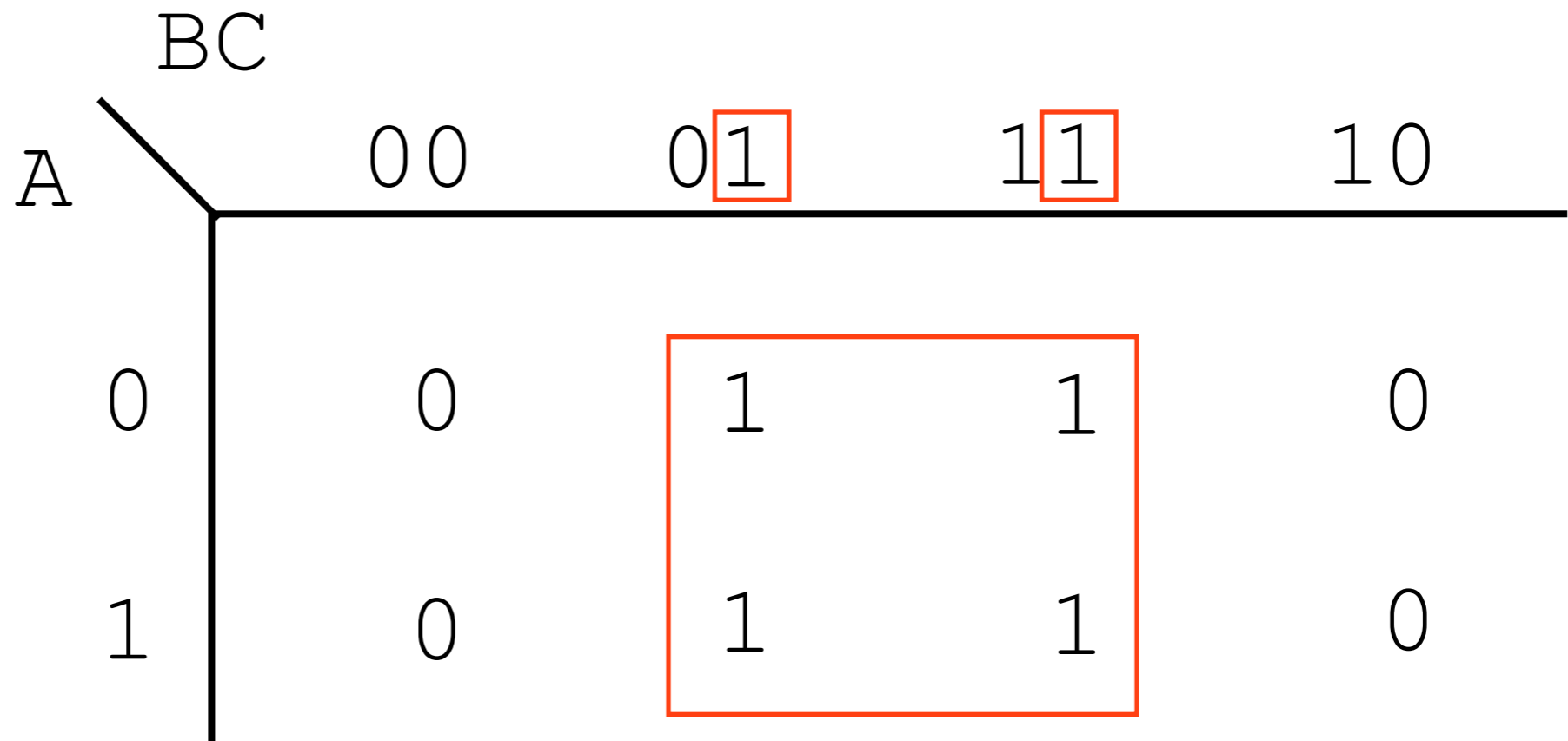

-Save the ones that stay the same in a group, discarding the rest

Another Three Variable Example

$$R = !A!B!C + !A!BC + !ABC + \\ !AB!C + A!B!C + AB!C$$

-Start with this formula


$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

-Build the truth table

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

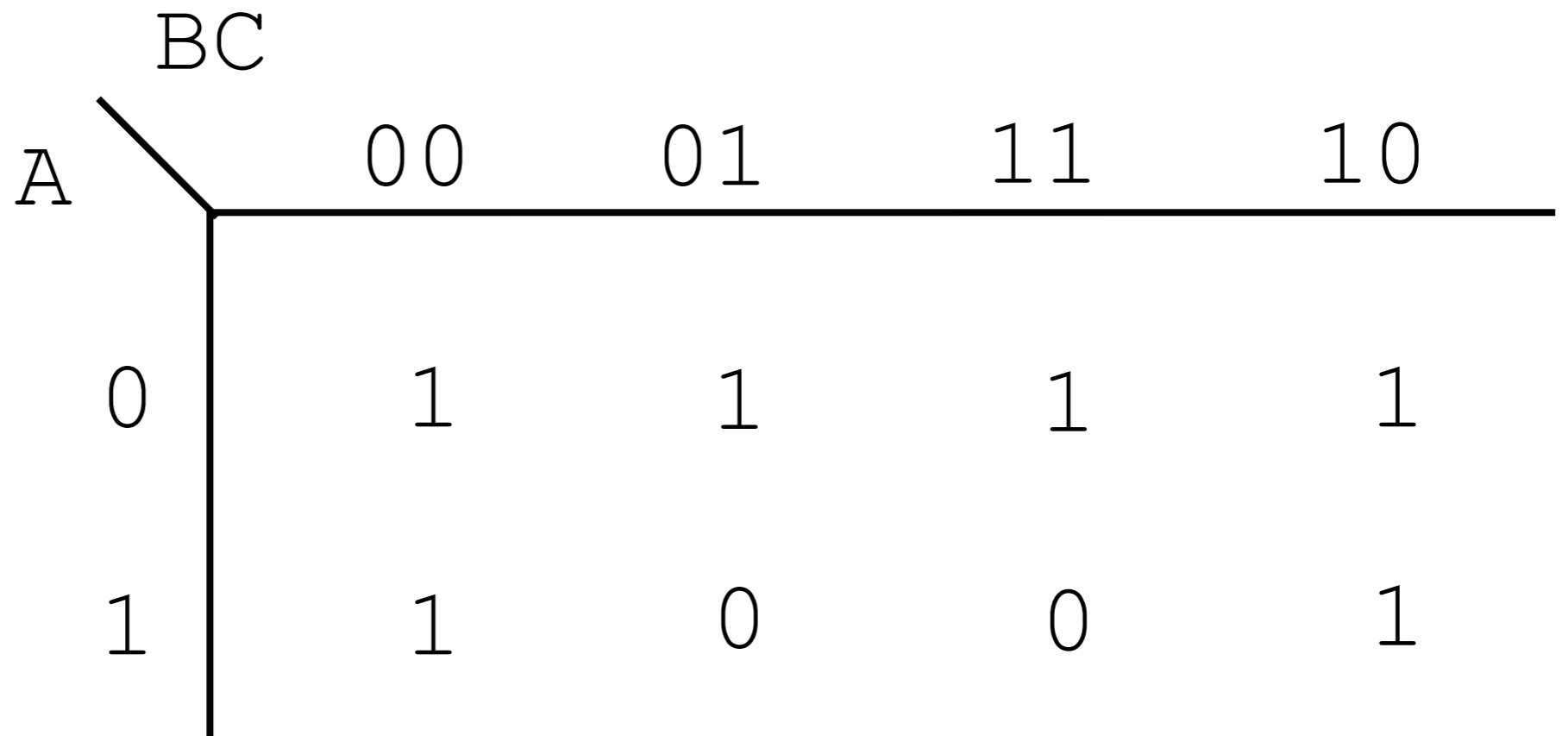

-Build the K-map

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

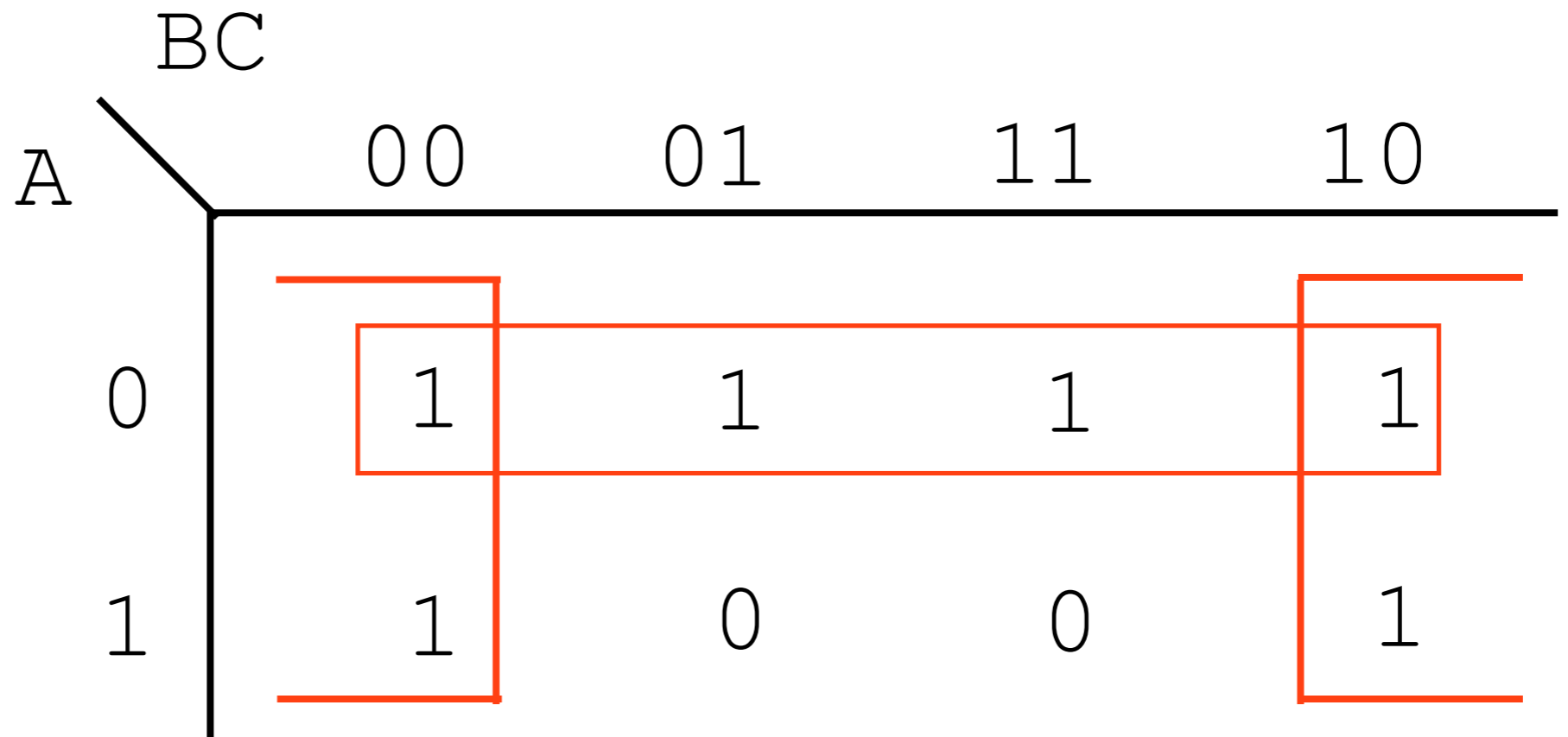

- Select the biggest groups possible
- Note that the values "wrap around" the table

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$


A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

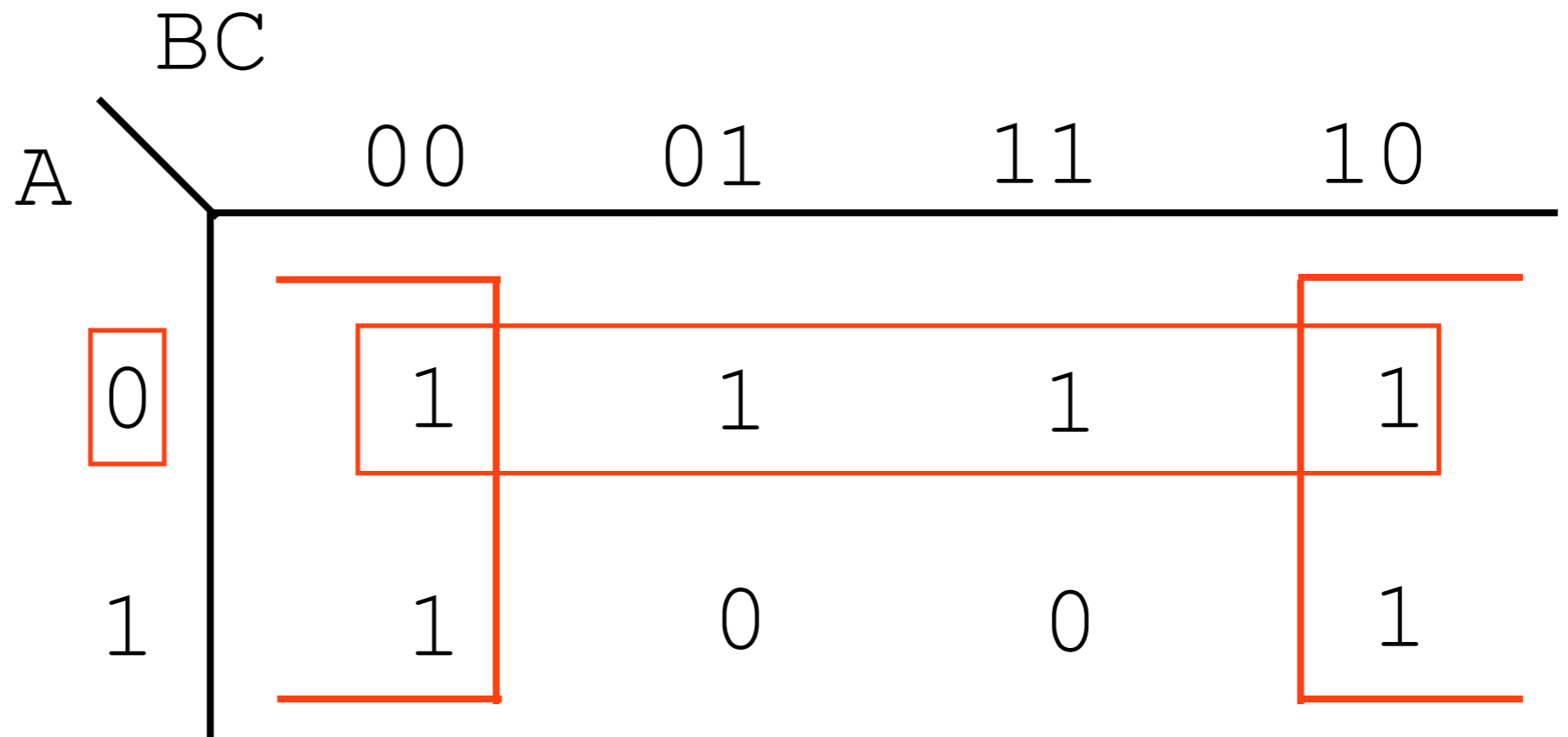

- Save the ones that stay the same in a group, discarding the rest
- This must be done for each group

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

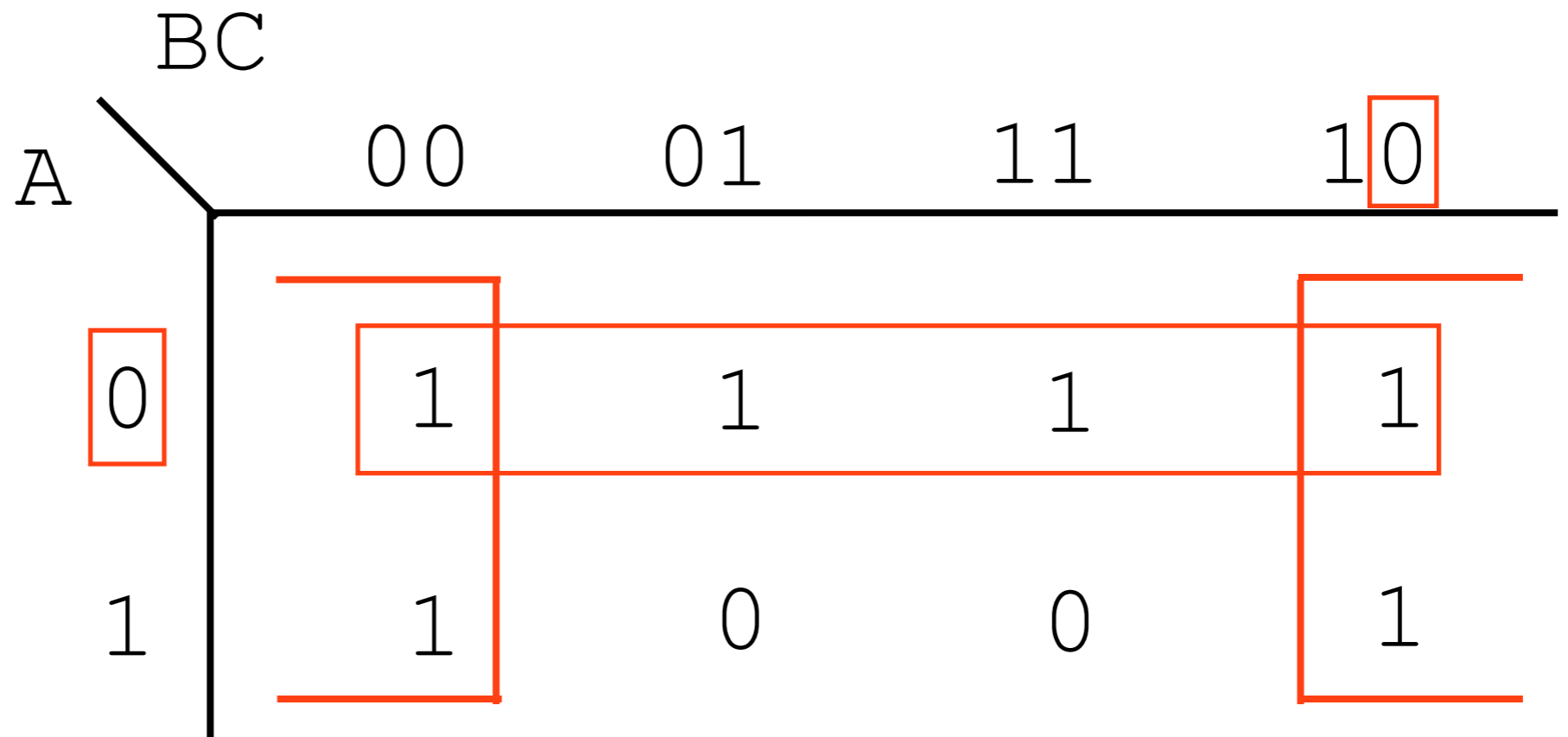


- Save the ones that stay the same in a group, discarding the rest
- This must be done for each group

$$R = !A!B!C + !A!BC + !ABC + !AB!C + A!B!C + AB!C$$

A	B	C	R
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$R = !A + !C$$

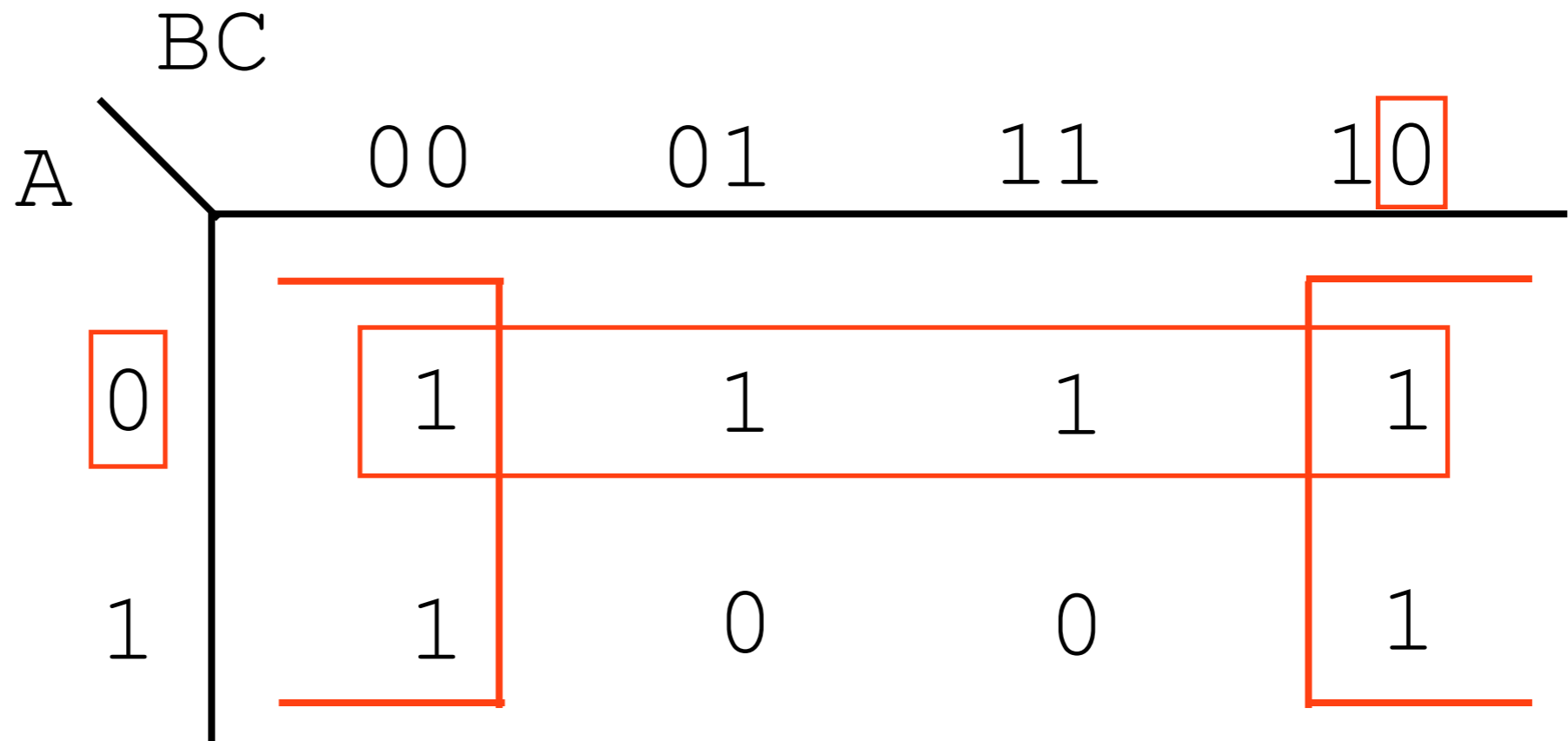

- Save the ones that stay the same in a group, discarding the rest
- This must be done for each group

Four Variable Example

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$


-Take this formula

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	1	0	1

-For space reasons, we go directly to the K-map

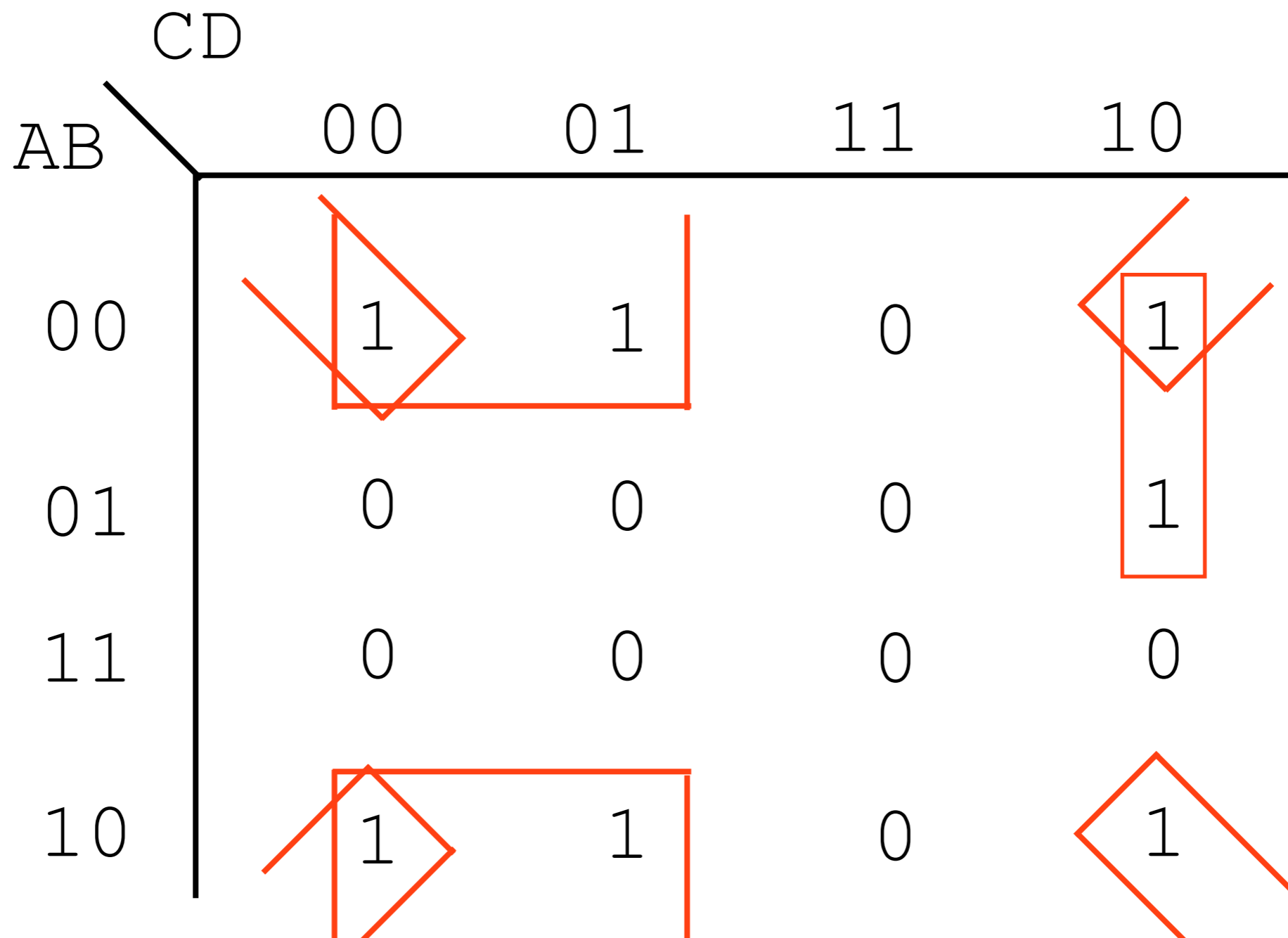
$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$



- Group things up
- The edges logically wrap around!
- Groups may overlap each other

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$


$$R = !B!C$$

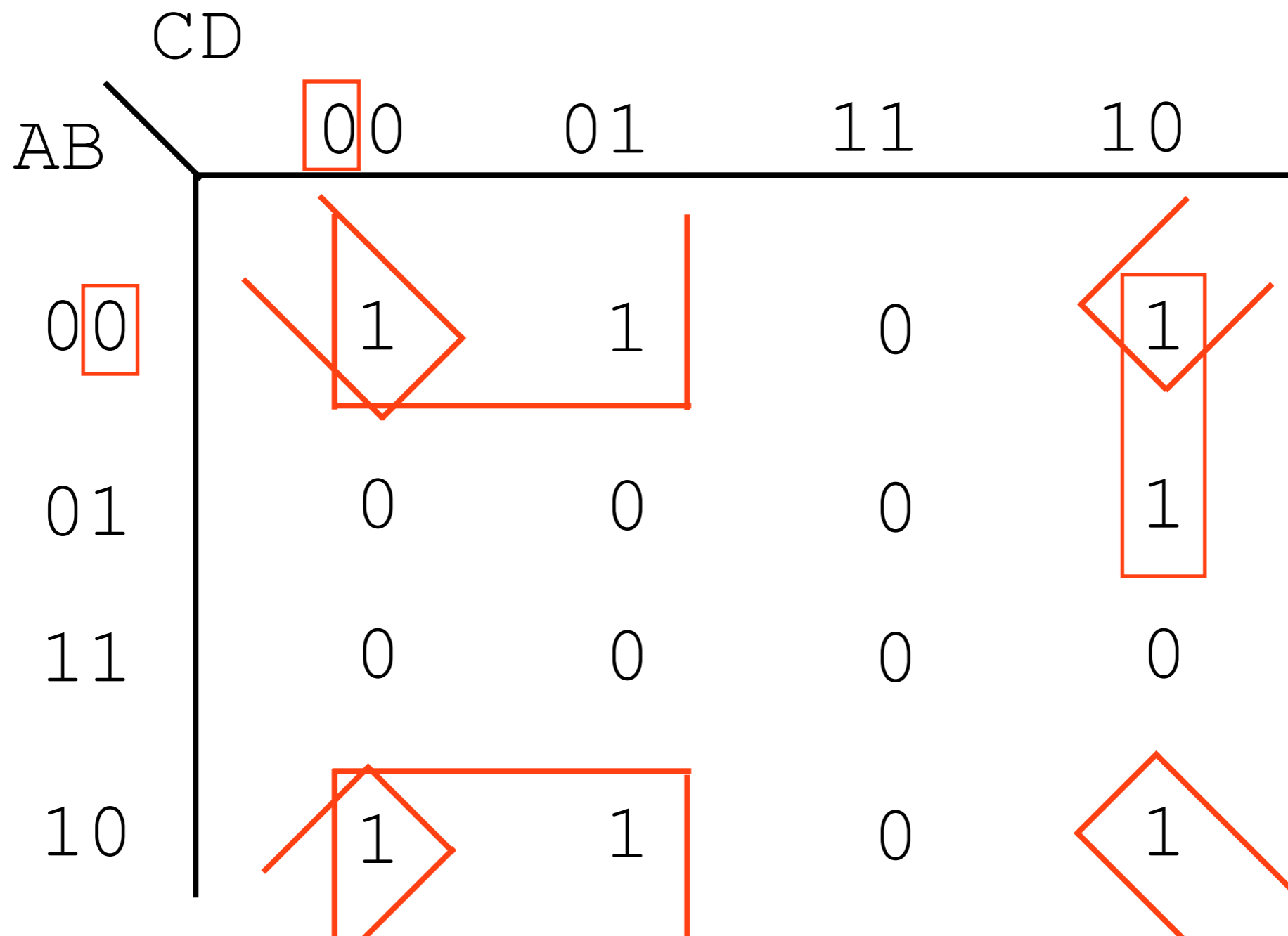

- Look at the bits that don't change
- First for the cube

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$


$$R = !B!C + !B!D$$

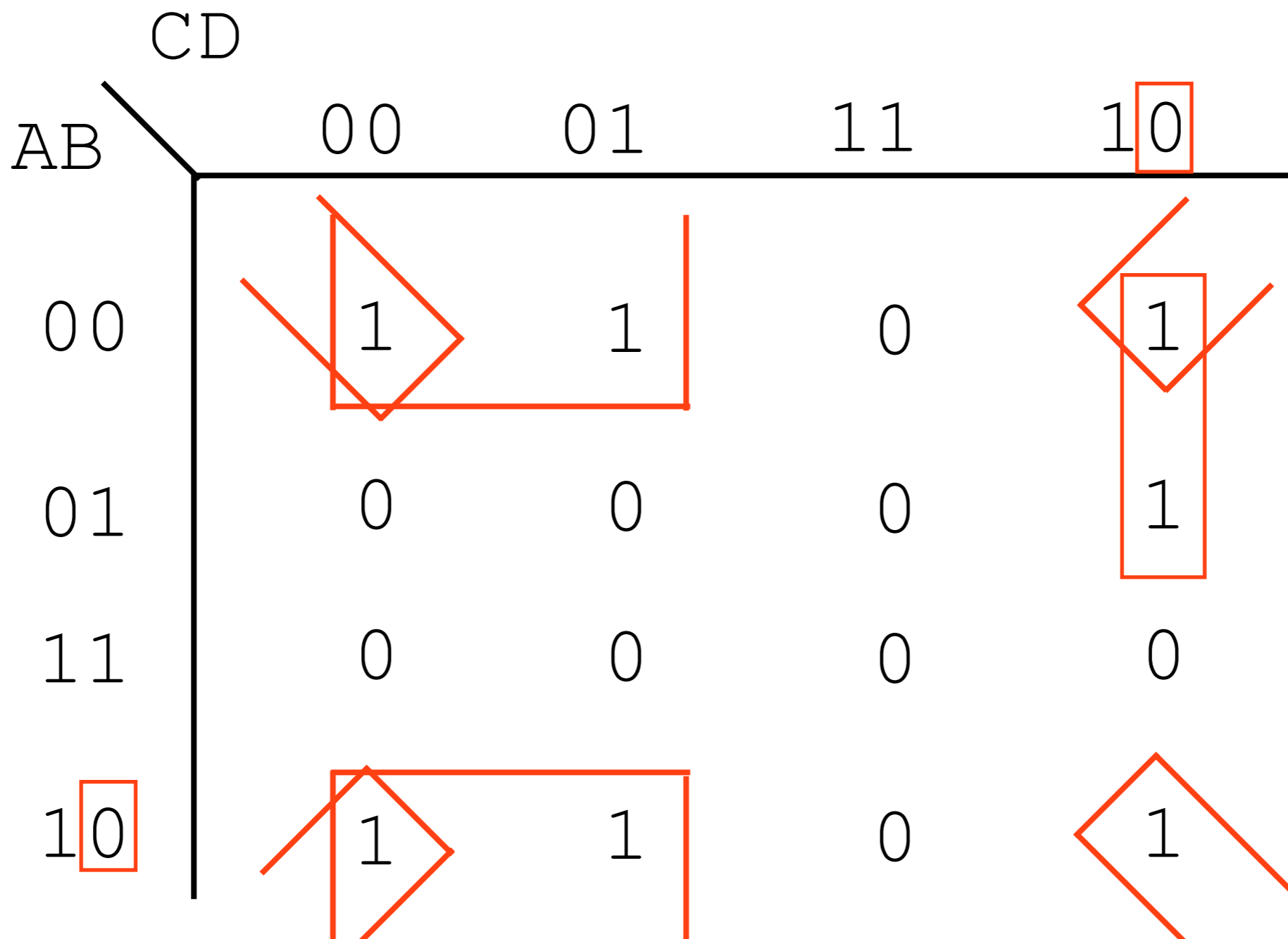

- Look at the bits that don't change
- Second for the cube on the edges

$$R = !A!B!C!D + !A!B!CD + !A!BC!D + !ABC!D + A!B!C!D + A!B!CD + A!BC!D$$

$$R = !B!C + !B!D + !AC!D$$

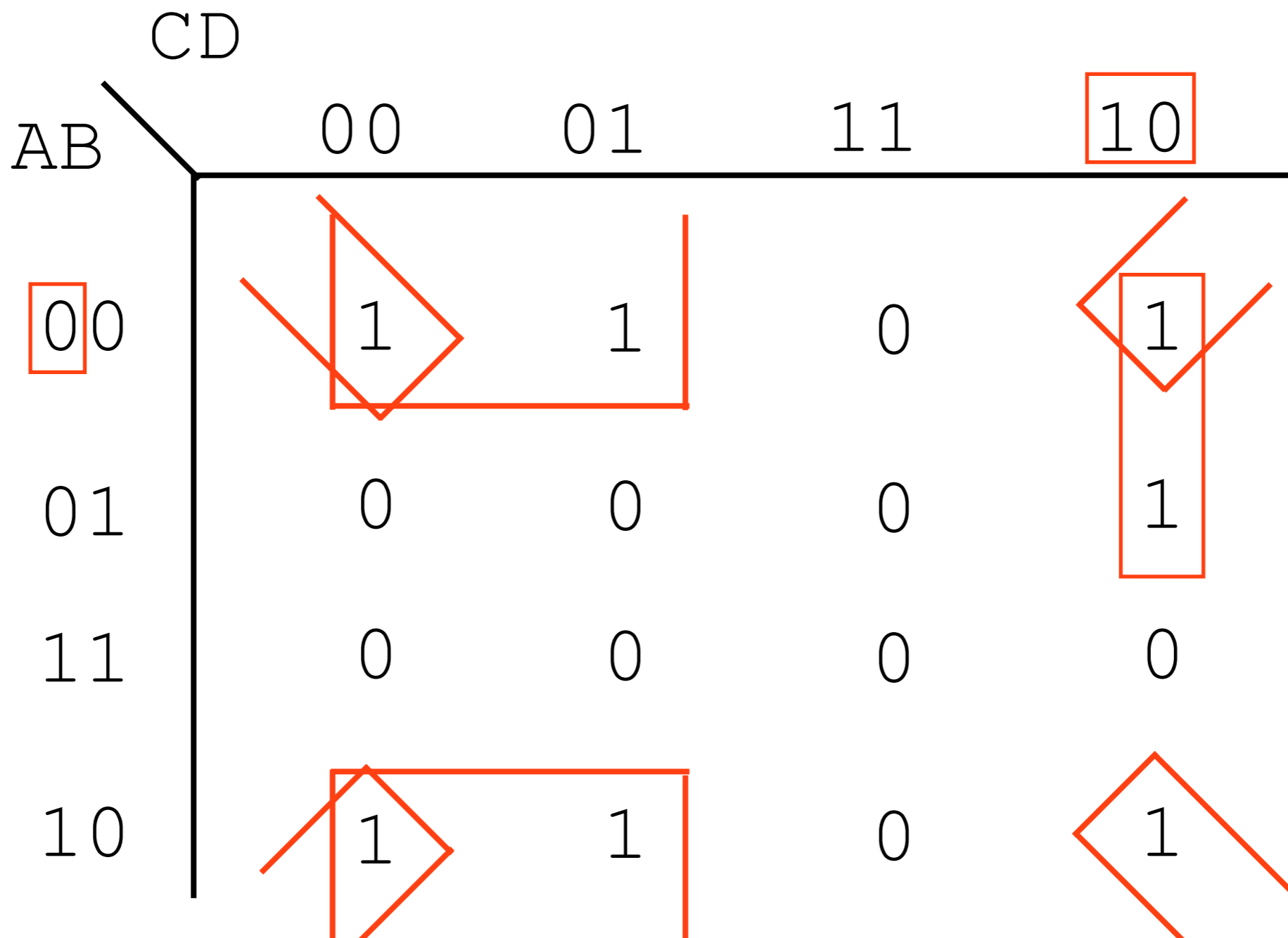

- Look at the bits that don't change
- Third for the line

K-Map Rules in Summary (I)

- Groups can contain only 1s
- Only 1s in adjacent groups are allowed (no diagonals)
- The number of 1s in a group must be a power of two (1, 2, 4, 8...)
- The groups must be as large as legally possible

K-Map Rules in Summary (2)

- All 1s must belong to a group, even if it's a group of one element
- Overlapping groups are permitted
- Wrapping around the map is permitted
- Use the fewest number of groups possible

Revisiting Problem

$$!A!BC + A!B!C + !ABC + !AB!C + A!BC$$

Revisiting Problem


$$R = \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

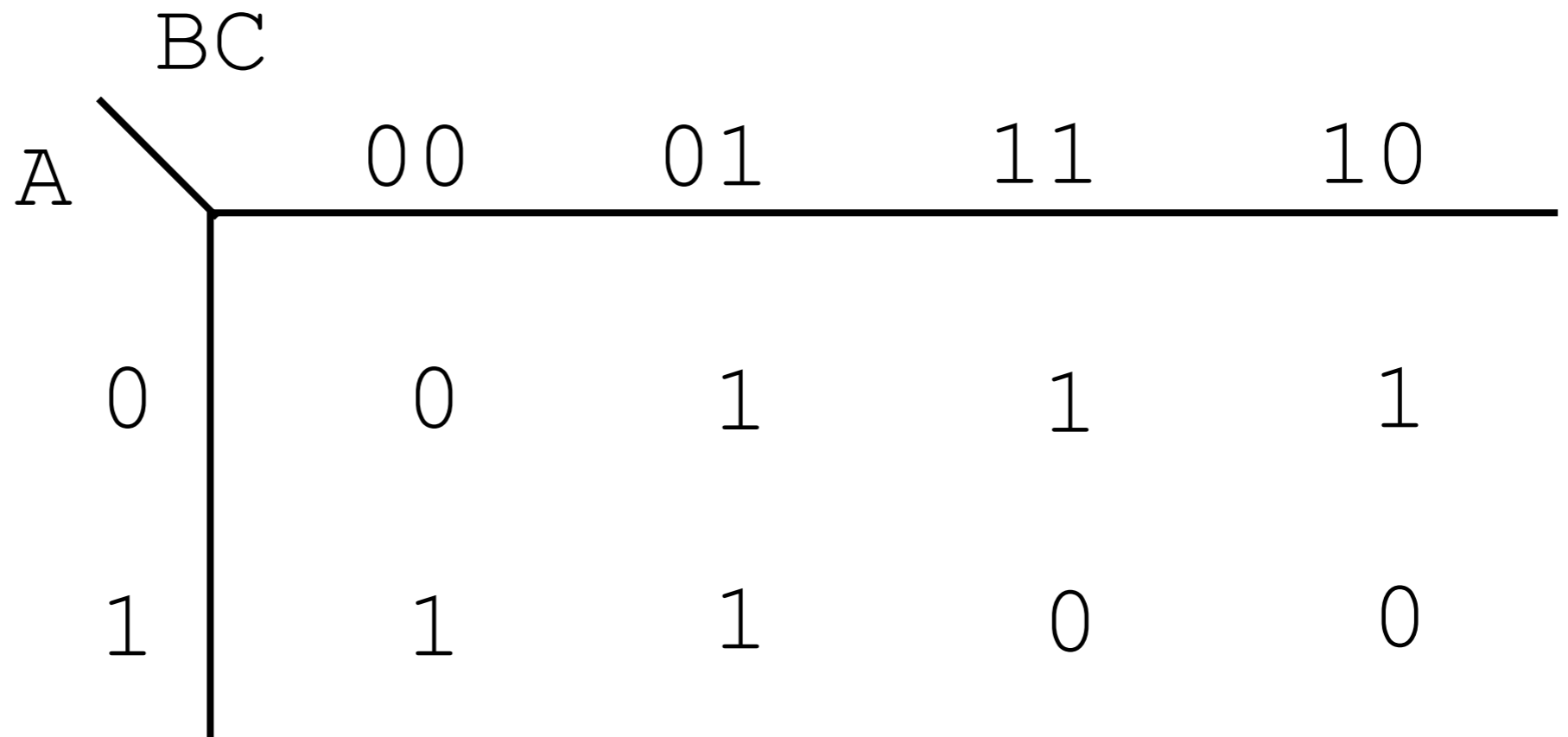


Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = !AC$$

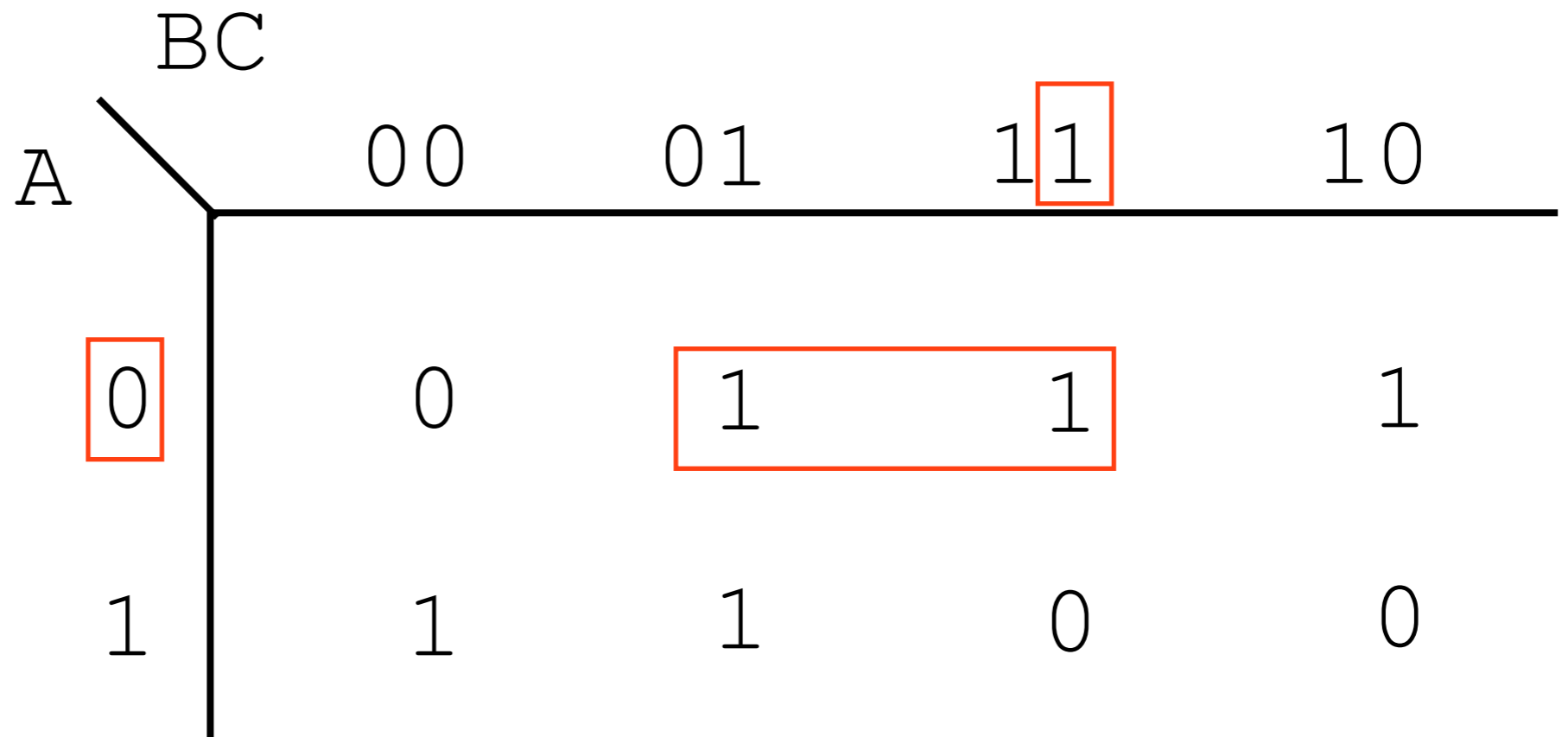


Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = !AC + A!B$$

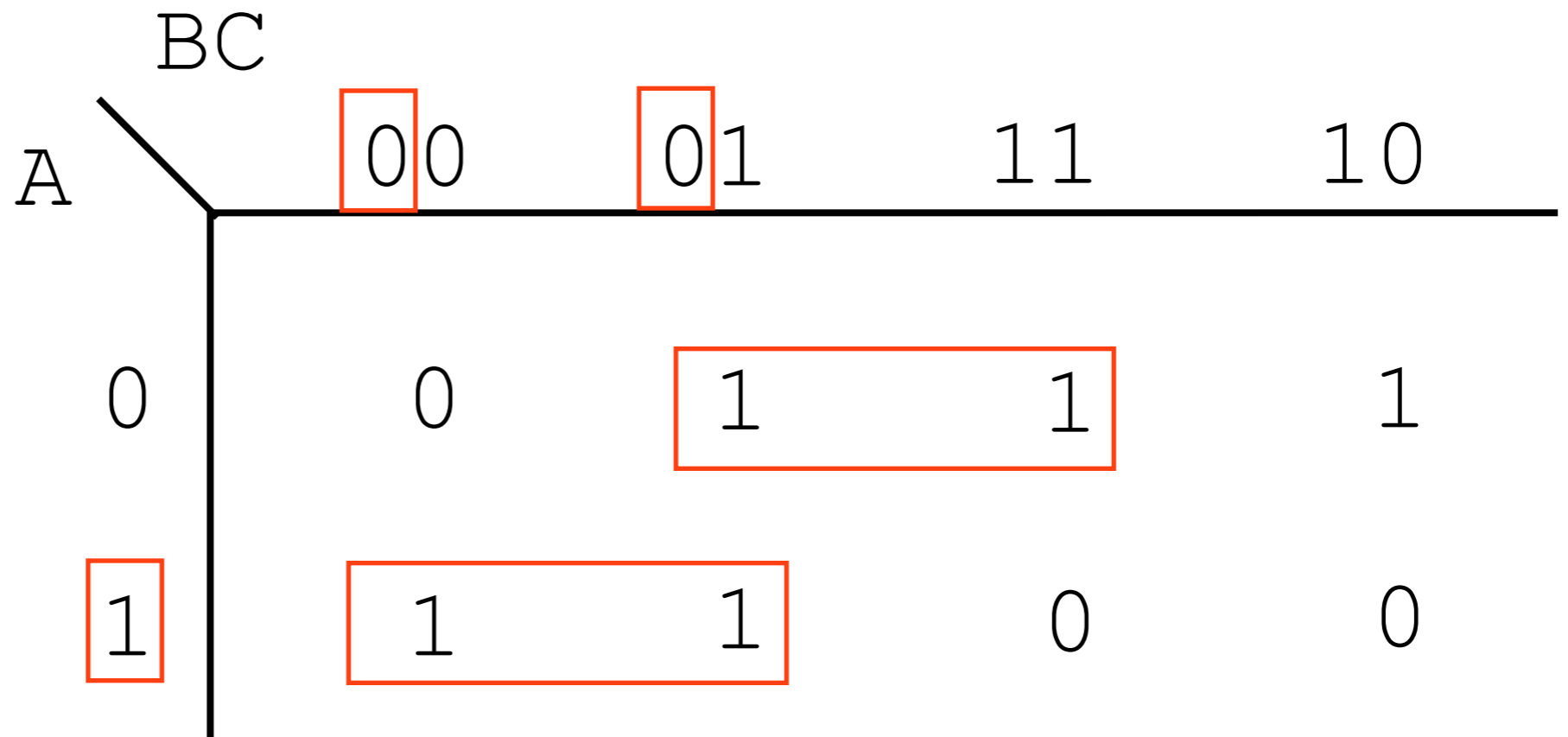


Revisiting Problem

$$R = !A!BC + A!B!C + !ABC + !AB!C + A!BC$$

A	B	C	R
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$R = !AC + A!B + !AB!C$$

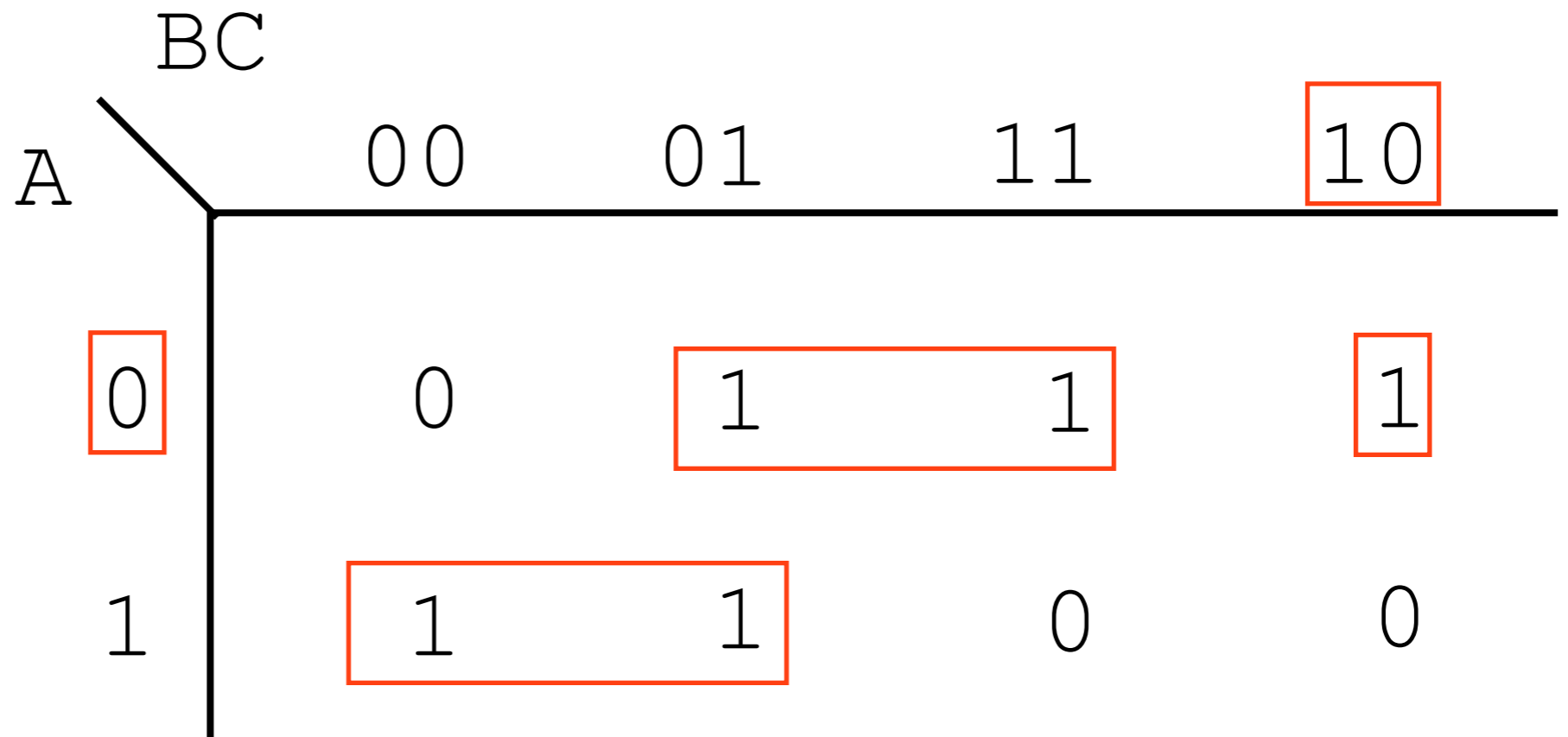

Difference

- Algebraic solution: $\neg BC + A\neg B\neg C + \neg AB$
- K-map solution: $\neg AC + A\neg B + \neg AB\neg C$
- Question: why might these differ?

Difference

- Algebraic solution: $\overline{B}C + A\overline{B}\overline{C} + \overline{A}B$
- K-map solution: $\overline{A}C + A\overline{B} + \overline{A}B\overline{C}$
- Question: why might these differ?
 - Both are *minimal*, in that they have the fewest number of products possible
 - Can be multiple minimal solutions

Difference

- Algebraic solution: $\overline{B}C + A\overline{B}\overline{C} + \overline{A}B$
- K-map solution: $\overline{A}C + A\overline{B} + \overline{A}B\overline{C}$
- Question: why might these differ?
 - Both are *minimal*, in that they have the fewest number of products possible
 - Can be multiple minimal solutions

Difference

Algebraic solution: $\neg BC + A\neg B\neg C + \neg AB$

K-map solution: $\neg AC + A\neg B + \neg AB\neg C$

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	1	0	0

-If we take our k-map from before with the grouping we chose, we get this particular solution

Difference

Algebraic solution: $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$

K-map solution: $\bar{B}C + A\bar{B}\bar{C} + \bar{A}B$

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	1	1	0	0

-If, however, we choose a different (also valid) grouping, we get the same solution as we did algebraically